

NAME: Himanshu Dixit

Batch: B10

ENROLL NO.: 21103262

Date _____

Page _____

ELECTRICAL SCIENCE - I (15B11EC111)

Tutorial Sheet - 2

Q.1. Power supplied by the VCCS : $i_d V_d$

$$\therefore i_d = 4V_c = 4(-2) = -8A$$

$$V_d = 2V$$

$$P_{VCCS} = -8 \times (2) = -16 \text{ watt} \quad \therefore \text{Power} = 16 \text{ W}$$

Q.2. (a) Current in R : $i = \frac{V_s}{R} = \frac{15}{5} = 3A$


$$\text{Power absorbed by resistor : } P = i^2 R = 9 \times 5 = 45 \text{ watt}$$

(b) Since neither V_s & nor R change and their is no effect in 'i' in R by changing i_s .

$$\therefore i = 3A$$

$$P = 45W$$

Q.3.

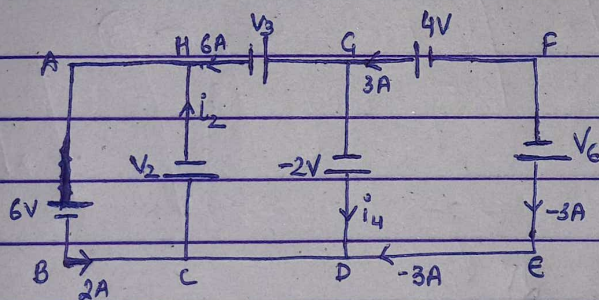

By KVL :

$$\text{In ABCHA : } -6 - V_2 = 0$$

$$V_2 = -6V$$

$$\text{In CDGHC : } +2 - V_3 + V_2 = 0$$

$$V_3 = 2 - 6 = -4V$$

$$\text{In DEFCD : } -V_6 + 4 - 2 = 0$$

$$V_6 = 2V$$

By KCL :


In node C : $i_2 = i_4 - 3 + 2$

$i_2 = i_4 - 1 \quad \text{--- (1)}$

In node G : $3 = 6 + i_4 \quad \text{--- (2)}$

$i_4 = -3 \text{ A}$

$i_2 = -4 \text{ A}$

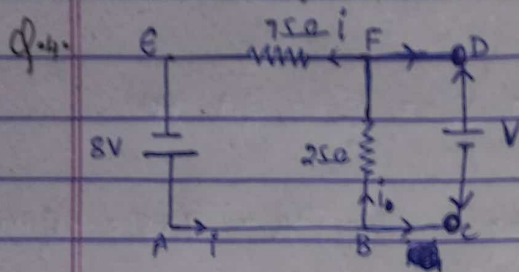

In ABFEA : $-25i_2 + 75i + 8 = 0$

$25i + 75i = 8 \quad \text{--- (1)} \quad \therefore i = \frac{8}{100} \text{ A}$

In BCDFB : $V + 25i = 0$
 $V = -25i \quad \text{--- (2)}$

In ABCDFEA : $V - 75i + 8 = 0$
 $V - 75i = -8 \quad \text{--- (3)}$
 $25i - 75i = -8$
 $i = \frac{-8}{-50} = \frac{4}{25} \text{ A}$

$V = 25i = 2 \text{ V}$


Q.5. (a) $R_{net} = 100 + 400 + 300 = 800 \Omega$

$i_{net} = \frac{V}{R_{net}} = \frac{12}{800} = \frac{3}{200} \text{ A}$

$V_2 = i_{net} R_2 = \frac{3}{200} \times 400 = 6 \text{ V}$

(b) $V_2 = -V_b$ (circuit are similar but voltage are opp.)
 $\therefore V_b = -6V$ ✓

Q.6.

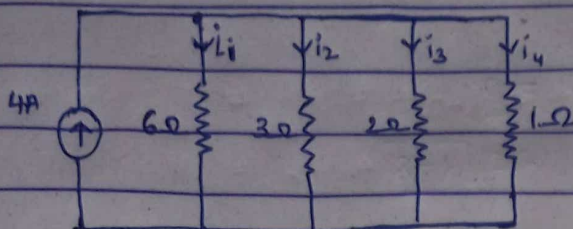

$$\frac{1}{R_{net}} = \frac{1}{6} + \frac{1}{3} + \frac{1}{2} + \frac{1}{1}$$

$$R_{net} = \frac{6}{6+3+2+1} = \frac{1}{2} \Omega$$

Current division : $I_x = R_{net} \times I_s$
 ~~$R_{net} \times$~~

$$i_1 = \frac{\frac{1}{2} \times 4}{6} = \frac{1}{3} A = 0.333 A \quad \checkmark$$

$$i_2 = \frac{\frac{1}{2} \times 4}{3} = \frac{2}{3} A = 0.666 A \quad \checkmark$$

$$i_3 = \frac{\frac{1}{2} \times 4}{2} = 1 A \quad \checkmark$$

$$i_4 = \frac{\frac{1}{2} \times 4}{1} = 2 A \quad \checkmark$$