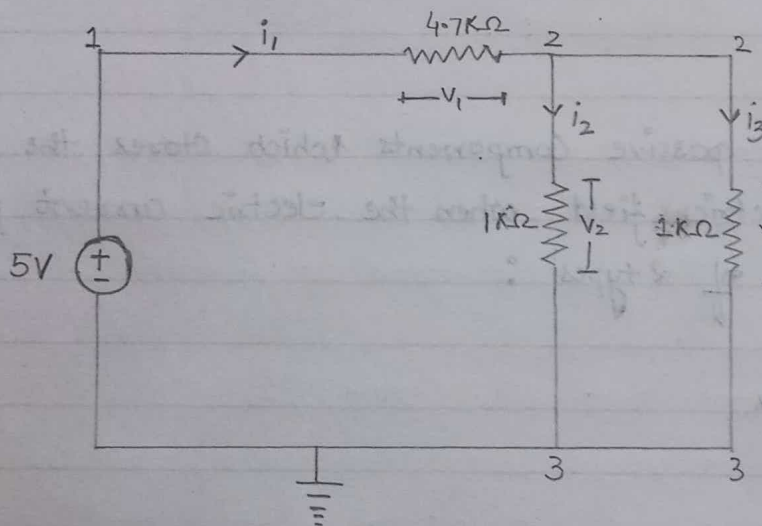


Fig. 1



(i) part

EXPERIMENT - 02

Aim :-

Verification of KVL &amp; KCL using a given circuit.

Apparatus Required :- (Multism live)

Multimeter (Digital), DC regulated power supply, bread board, Two  $1k\Omega$  resistors, one  $4.7k\Omega$  resistor

Theory :-

There are two types of Kirchhoff's law :

- (a) Kirchhoff's Voltage law - KVL states that the algebraic sum of all the voltages encountered as one goes around complete loop is zero.

$$V_1 - R_1 I_1 - R_2 I_2 = 0$$

(as shown in Fig 1)

$$R_2 I_2 - R_3 I_3 = 0$$

$$V_1 - R_1 I_1 - R_3 I_3 = 0$$

- (b) Kirchhoff's Current law - KCL states that the algebraic sum of current entering to the point of Node and current leaving to that Node is equal to zero.


$$I_1 - I_2 - I_3 = 0 \quad (\text{as shown in Fig.1})$$

Observation Table :-

Measured current and potential :

Teacher's Signature: \_\_\_\_\_

# Experiment - 02

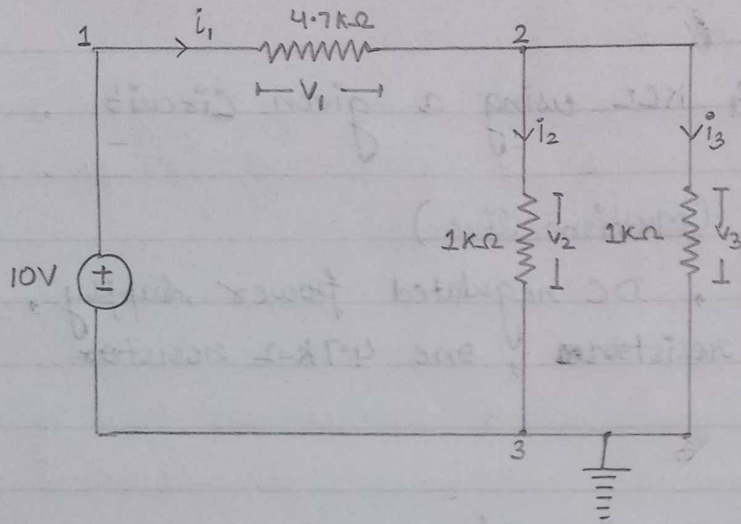

(ii) part

Observation Table :-



Input Voltage $V$ (volts)	Voltage across $R_1$ ( $V_1$ ) V	Voltage across $R_2$ ( $V_2$ ) (mV)	Voltage Across $R_3$ ( $V_3$ ) (mV)	Current across $R_1$ (mA)	Current across $R_2$ (mA)	Current Across $R_3$ (mA)
5 V	4.526 V	0.480 mV	0.480 mV	0.961 mA	0.480 mA	0.480 mA
10 V	9.04 V	0.961 mV	0.961 mV	1.9231 mA	0.961 mA	0.961 mA

Calculation :-(i) Calculation for 1<sup>st</sup> part :

$$R_1 = 4.7 \text{ k}\Omega, R_2 = R_3 = 1 \text{ k}\Omega$$

$$4.7i_1 + i_2 = 5 \quad \times 2$$

$$i_1 - 2i_2 = 0 \quad \text{--- (1)}$$

$$9.4i_1 + 2i_2 = 10 \quad \text{--- (2)}$$

+ \_\_\_\_\_

$$10.4i_1 = 10 \rightarrow i_1 = 0.961 \text{ mA} \text{ \& } i_2 = 0.480 \text{ mA}$$

$$\text{Voltage Across } R_1 : V_1 = i_1 R_1 = 4.5 \text{ V}$$

$$\text{Voltage Across } R_2 : V_2 = i_2 R_2 = 0.480 \text{ mV}$$

$$\text{Voltage Across } R_3 : V_3 = i_3 R_3 = 0.480 \text{ mV}$$

At node 2 :  $I_1 - I_2 - I_3 = 0$  hence, KCL is proved.

& Similarly, Total Voltage (sum) = 0 hence, KVL is proved.  
 $(5 - V_1 - V_2) = 5 - 4.5 - 0.48 \approx 0$

(input voltage - Total sum of voltage drop) should be zero

(ii) Calculation for 2<sup>nd</sup> part :

$$R_1 = 4.7k\Omega, R_2 = R_3 = 1k\Omega$$

$$4.7i_1 + i_2 = 10 \quad \times 2$$

$$i_1 - 2i_2 = 0 \quad \text{--- ①}$$

$$9.4i_1 + 2i_2 = 20 \quad \text{--- ②}$$

+

$$i_1 = \frac{20}{10.4} = 1.92 \text{ mA}, \quad i_2 = 0.961 \text{ mA}$$

$$\text{Voltage across } R_1 : V_1 = i_1 R_1 = 9.04 \text{ V}$$

$$\text{voltage across } R_2 : V_2 = i_2 R_2 = 0.961 \text{ mV}$$

$$\text{voltage across } R_3 : V_3 = i_3 R_3 = 0.961 \text{ mV}$$

$$\text{At node 2 : } i_1 - i_2 - i_3 = 0, \text{ KCL Proved}$$

$$\text{In first loop : } (V_1 + V_2 - 10) \text{ should be } 0$$

$$9.04 + 0.96 - 10 = 0, \text{ hence, KVL Proved.}$$

Result :-

- (i) At node Incoming current is found to be equal to outgoing current.
- (ii) The total input voltage is found to be equal to the total voltage drop in the circuit.

Precaution :-

- (i) All connection should be tight & correct.
- (ii) Switch off supply when not in use.
- (iii) Reading should be taken carefully.

Learning Outcomes :-

KCL & KVL are very important in solving the circuits where direct formula can't be applied.

Teacher's Signature: \_\_\_\_\_



